

voltage, usually in the range of 3.3 to 3.6 V. Since the USB power supply is in the range of 4.5 to 5.25 V, we need a low drop voltage regulator. Advantages of this solution are:

- Clean solution, fast transitions on D+ and D-.
- Good noise immunity for signal input.

Disadvantages:

- Low drop regulators are often expensive and harder to obtain.
- Many AVR's are not specified for the required clock rates at supply voltages below 4.5 V.
- Other chips on the board may not be specified for 3.3 V.

Note that using low-drop regulators LE33CZ, or even worse, LM1117S33, imposes additional supply current (quiescent current) that violates the 500 μ A limit for USB standby. Because the 1.5 k Ω pull-up contributes 200 μ A, only 299 μ A are allowed for the regulator if the ATmega is in its deep standby drawing less than 1 μ A. For compliance with the USB standard, very low-power low-drop regulators like [TPS71533DCK](#) are required. Small quantities can be obtained from [Texas Instruments](#) as samples for free.

Another variation of this approach is to reduce the supply voltage with two rectifier diodes in series. This gives roughly a drop of 1.2 to 1.4 V, usually enough to make things work. The missing regulation may be problematic for analog circuitry or if you use the ADC. It depends on the power consumption of the device and the PC side voltage supply stability.

Additional advantages:

- Low cost, easily orderable devices.
- No quiescent current, makes this solution ideal for USB compliant standby mode.

Additional disadvantages:

- No regulation, only voltage step-down.
- Unregulated voltage problematic for analog circuitry, ADC usage, and maybe attached digital circuitry.

Solution B: Level conversion on D+ and D-




Instead of reducing the AVR's power supply, we can limit the output voltage on D+ and D- with Zener diodes. We recommend 3.6 V low power types, those that look like 1N4148 (usually 500 mW or less). Low power types are required because they have less capacitance and thus cause less distortion on the data lines. And 3.6 V is better than 3.3 V because 3.3 V diodes yield only ca. 2.7 V in conjunction with an 1.5 k Ω (or more exactly 10 k Ω) pull-up resistor. With 3.3 V diodes, the device may not be detected reliably.

If you use Zener diodes for level conversion, please measure the voltage levels to make sure that the diodes you have chosen match the requirements.

Advantages of the Zener diode approach:

- Low cost.
- Easy to obtain.
- Entire design can be at 5 V.
- AVR can be clocked at high rates.

Disadvantages:

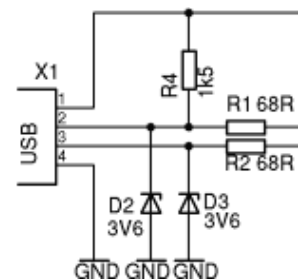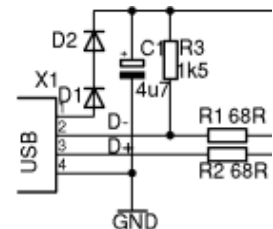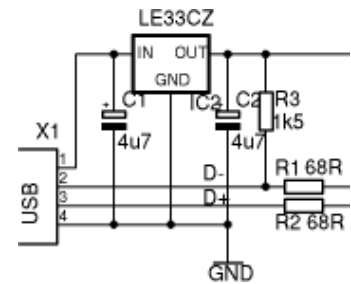

- Not a clean solution, a compromise between all parameters must be found.
- Zener diodes come with a broad range of characteristics, especially at low currents, results may not be reproducible.
- High currents when sending high-level.
- High level is different for signaling and in idle state because signaling uses high currents to drive the diodes while idle state is driven by a 1.5 kΩ pull-up resistor.

Which clock rate should I choose?

V-USB can currently handle clock rates of 12 MHz, 12.8 MHz, 15 MHz, 16 MHz, 16.5 MHz, 18 MHz and 20 MHz. These clock rates are *precise*! A crystal with 11.9 MHz won't work! Only the 16.5 MHz and 12.8 MHz variants allow a deviation of up to 1%. They are therefore suitable for RC oscillators. 16.5 MHz is suitable for devices which can derive a 16 MHz clock from an RC oscillator (e.g. ATtiny25/45/85 and ATtiny26), 12.8 MHz can usually be reached by calibrating the 8 MHz RC oscillator. Calibration of the RC oscillator is described at [examples](#).

The driver uses different code in the assembler routines for each clock rate. All assembler modules should be equally reliable. Your decision can therefore be based on the following criteria:

- Do you want to use the RC oscillator? Then you need the 16.5 MHz module.
- Is code space very tight? Then we recommend the 16 MHz or 20 MHz module, these have the least code size.
- Is the AVR powered at low voltage? Then we recommend 12 MHz for reliable operation.
- If you want to include CRC checks on USB transfers (available in vusb-releases since 2009-03-23) use 18 MHz.
- Do other parts of the code or hardware require a particular clock rate? Well, then you have no choice and are lucky if the rate is supported by V-USB.

Designs based on the RC oscillator need calibration. [EasyLogger](#) starting with version 2008-02-28 includes code for auto-calibration based on the USB frame clock. This code is now also included in directory `libs-device` of the driver package.

page revision: 24, last edited: 29 Oct 2011, 17:09 (1543 days ago)

[Edit](#) [Tags](#) [History](#) [Files](#) [Print](#) [Site tools](#) [+ Options](#)

Powered by Wikidot.com

[Help](#) | [Terms of Service](#) | [Privacy](#) | [Report a bug](#) | [Flag as objectionable](#)

Unless otherwise stated, the content of this page is licensed under [Creative Commons Attribution-ShareAlike 3.0 License](#)

Other interesting sites



**Scion: Monsters and Mosh
Pits**



Хроника Убийцы Короля



**Electromagnetic
(Hyper)Sensitivity**

Causes of Electro Smog, EMF and
Wireless Devices



Connors Campaigns

My dashboard for RPGs, Music,
Sports, and more.